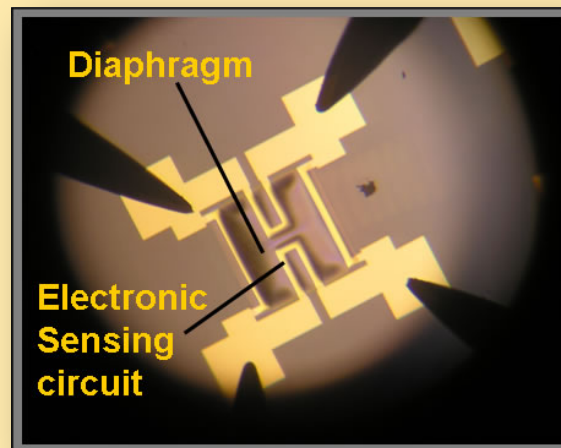


# WHEATSTONE BRIDGE OVERVIEW



# Unit Overview

This Wheatstone Bridge Overview provides information on the electronic circuitry of a Wheatstone bridge.

This overview will help you to understand how a Wheatstone bridge is used for sensing changes in pressure when used in a micro pressure sensor.

# Objectives

- ❖ Define the variable components of the Wheatstone bridge
- ❖ Describe how the Wheatstone bridge works

# Introduction to Wheatstone Bridge


- ❖ An electrical circuit design dating back to early 1800's
- ❖ Named for its most famous user, Sir Charles Wheatstone who
  - ▣ never claimed to have invented it, but did develop multiple uses for it
  - ▣ called the circuit a “Differential Resistance Measurer”
- ❖ Invented by Samuel Hunter Christie (1784-1865)
- ❖ One of the most sensitive and precise methods of measuring small changes in resistance through its use of transducers.
- ❖ Widely used today in macro and micro-sized sensors



*Sir Charles Wheatstone*  
National Portrait Gallery, London
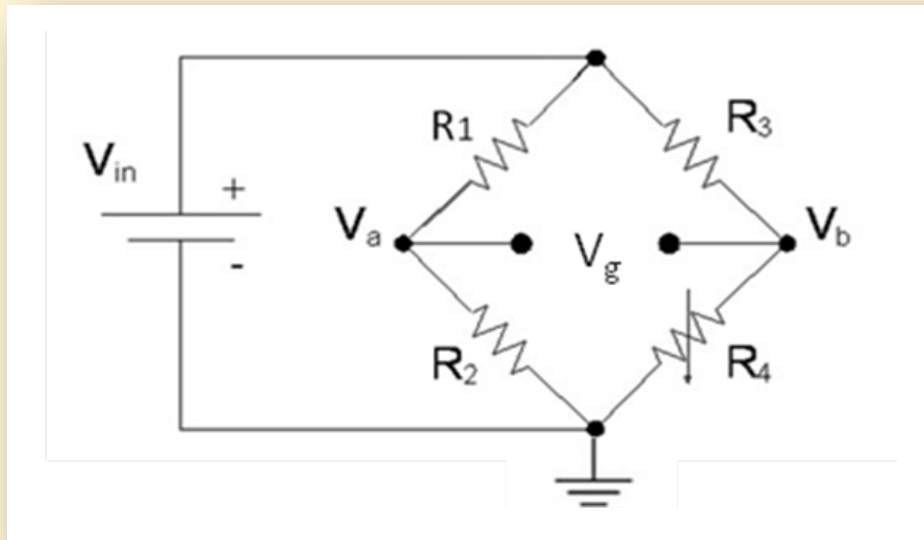
# The Wheatstone Bridge

- ❖ A simple circuit used to measure small changes in resistance of a transducer.
- ❖ Classic configuration consists of four resistors
  - ▣ Three fixed value and one variable value
  - ▣ Variable resistor is the sensing element (transducer) (See  $R_4$  in diagram below)
  - ▣ Resistance of the variable resistor changes due to a change in an environmental factor such as stress, pressure, or temperature




*Basic Wheatstone bridge Configuration with one transducer or sensing element ( $R_4$ )*
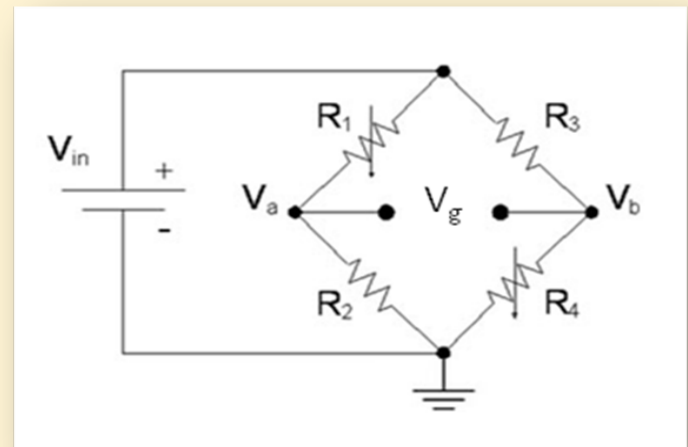
# The Wheatstone Bridge – 2 Variable Resistors

- ❖ Maximized effect of the input
- ❖ Provides the largest voltage variation as a function of the changing input
- ❖ Has 2 fixed resistors & 2 variable resistors (transducers/sensing elements)
- ❖ DC voltage source ( $V_{in}$ ) such as a battery or power supply
- ❖ Output voltage ( $V_g$ ) represents the difference in the transducers' resistance values to the reference resistance of the bridge configuration
- ❖ Design allows for the measurement of very small changes in the environmental factor that affects the transducers while greatly suppressing electrical noise and thus improving the “signal to noise ratio”

*Basic Wheatstone Bridge Configuration with two transducers or sensing elements ( $R_1$  and  $R_4$ )*




# Background Circuits

- ❖ There are three concepts discussed here which are needed to understand Wheatstone bridges:
  - ▣ Resistor voltage dividers
  - ▣ Ohm's Law ( $I=V/R$ )
  - ▣ Kirchhoff's Circuit Laws

# Resistor Voltage Dividers

- ❖ Diagram below is made up of two resistors labeled  $R_1$ ,  $R_2$ , and a power supply  $V_{in}$  (battery).
- ❖ Electron flow or current  $I_{in}$  (measured in Amperes (A)) travels from the negative terminal of the battery through the resistors to the positive terminal of the battery.

*Resistive Voltage Divider*

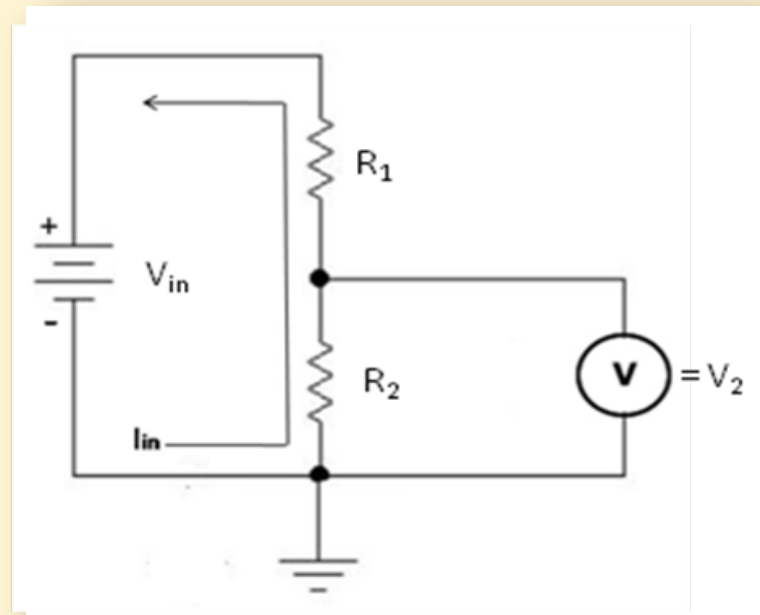



# Ohm's Law


- ❖ Ohm's Law determines the voltage drop across a resistor if the resistance  $R$  and current  $I$  are both known.
- ❖ Ohm's Law states:  $V = IR$ 
  - ▣ where  $V$  is the voltage across a resistor  $R$  that has current  $I$  flowing through it
- ❖ In the Resistive Voltage Divider circuit to the right, the voltage drop,  $V_1$  across resistor  $R_1$  is

$$V_1 = I_{in} R_1$$

- ❖ The voltage drop,  $V_2$  across resistor  $R_2$  is

$$V_2 = I_{in} R_2.$$

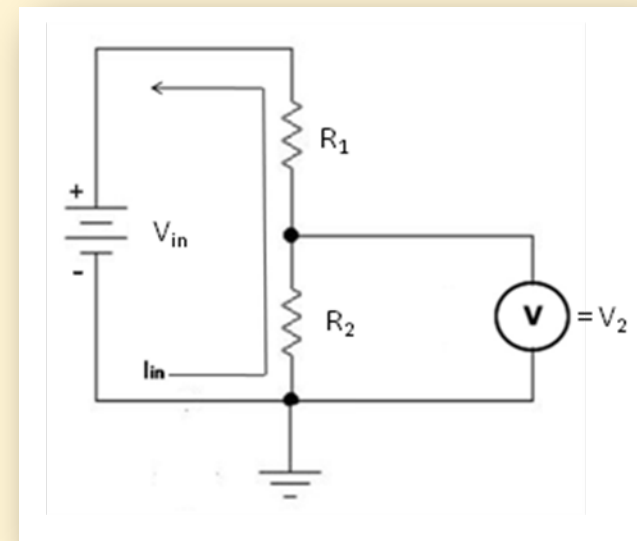- ▣ A voltmeter measures across  $R_2$  with one lead at ground and the other connected between  $R_1$  and  $R_2$



*Resistive Voltage Divider*

# Ohm's Law cont...

Let's put some numbers to this Voltage divider circuit and check out our calculations.


Using Ohm's Law, calculate  $I_{in}$ ,  $V_1$  and  $V_2$

$$I_{in} = \frac{V_{in}}{R_t}$$

$I_{in}$  is the current which flows through the circuit

$V_{in}$  is the voltage applied to the circuit

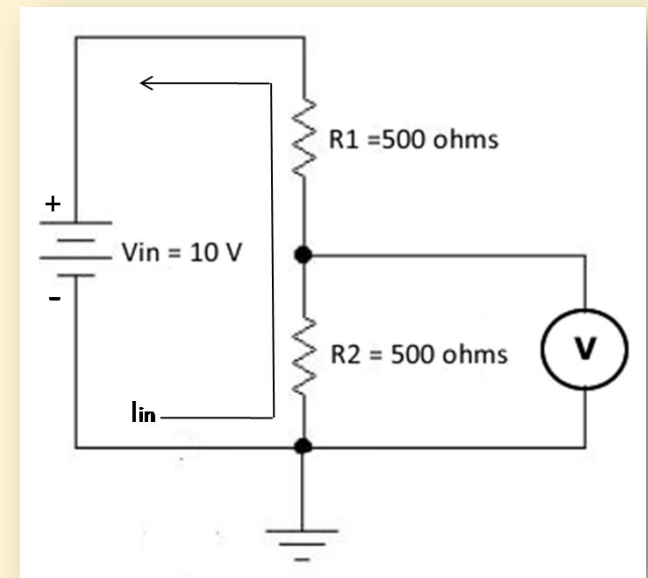$R_t$  is the total resistance that the current flows through



Now try it!

# Ohm's Law cont...

Let's see how you did:

The total circuit resistance  $R_t = R_1 + R_2$


$$I_{in} = \frac{V_{in}}{R_t} = \frac{10\text{volts}}{R_1 + R_2} = \frac{10\text{volts}}{500\Omega + 500\Omega} = \frac{10\text{volts}}{1000\Omega} = \frac{10\text{volts}}{1k\Omega} = 10mA$$

The voltage drop,  $V_1$  across resistor  $R_1$  is

$$V_1 = I_{in}R_1 \text{ or } 10mA * 500\Omega = 0.01A * 500\Omega = 5V$$

The voltage drop,  $V_2$  across resistor  $R_2$  is
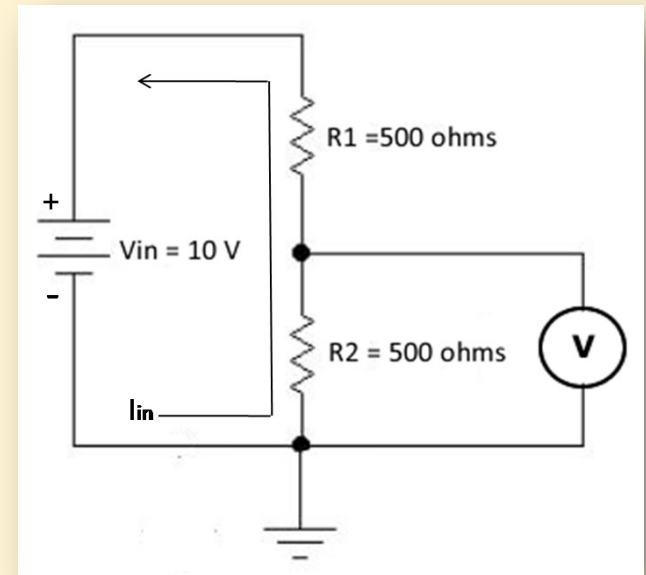
$$V_2 = I_{in}R_2 \text{ or } 10mA * 500\Omega = 0.01A * 500\Omega = 5V$$



# Kirchoff's Law

Kirchhoff's voltage law, states that the sum of the voltage drops across a collection of resistors arranged in series within a circuit is equal to the applied voltage ( $V_{in}$ ).

$$V_{in} = I_{in}R_1 + I_{in}R_2 = I_{in}(R_1 + R_2)$$

or

$$V_{in} = V_1 + V_2$$

Notice that the previous problem shows this to be true:

$$10 \text{ v } (V_{in}) = 5 \text{ v } + 5 \text{ v}$$

# Kirchoff's Law cont...

The voltage drop across a specific resistor in series with other resistors is the fraction of that resistor to the sum of the series resistors, multiplied by the applied voltage.

The formula is derived on the right.

Applying the values of the previous circuit, we get:

$$V_2 = \frac{500\Omega}{500\Omega + 500\Omega} 10V = 5V$$

$$I_{in} = \frac{V_{in}}{R_1 + R_2}$$

$$V_2 = I_{in} R_2 = \frac{V_{in}}{R_1 + R_2} R_2$$


$$V_2 = \frac{R_2}{R_1 + R_2} V_{in}$$

# Kirchoff's Law cont...

Wheatstone bridge has two such voltage dividers connected in parallel

Analysis of the *resistive voltage divider* circuit can be applied to the Wheatstone bridge circuit.

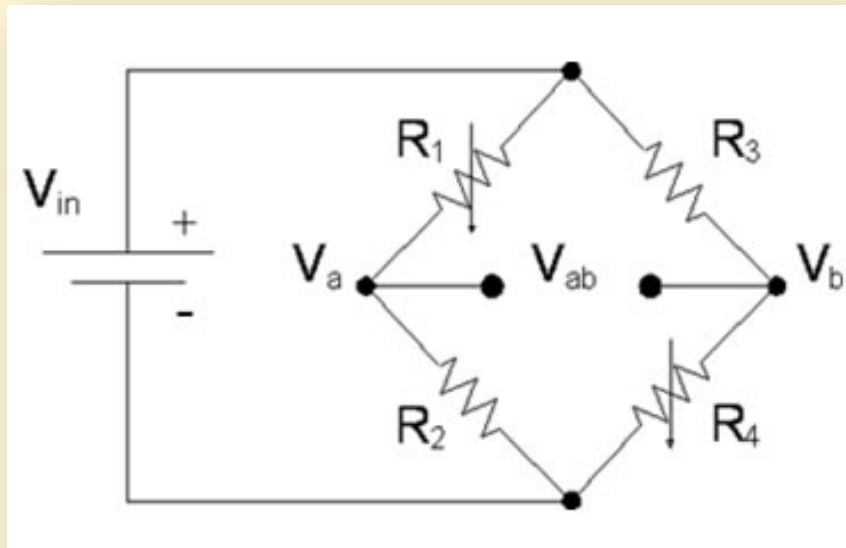
Identify the two voltage divider circuits in the circuit below,



*Wheatstone bridge with 2 variable resistors*
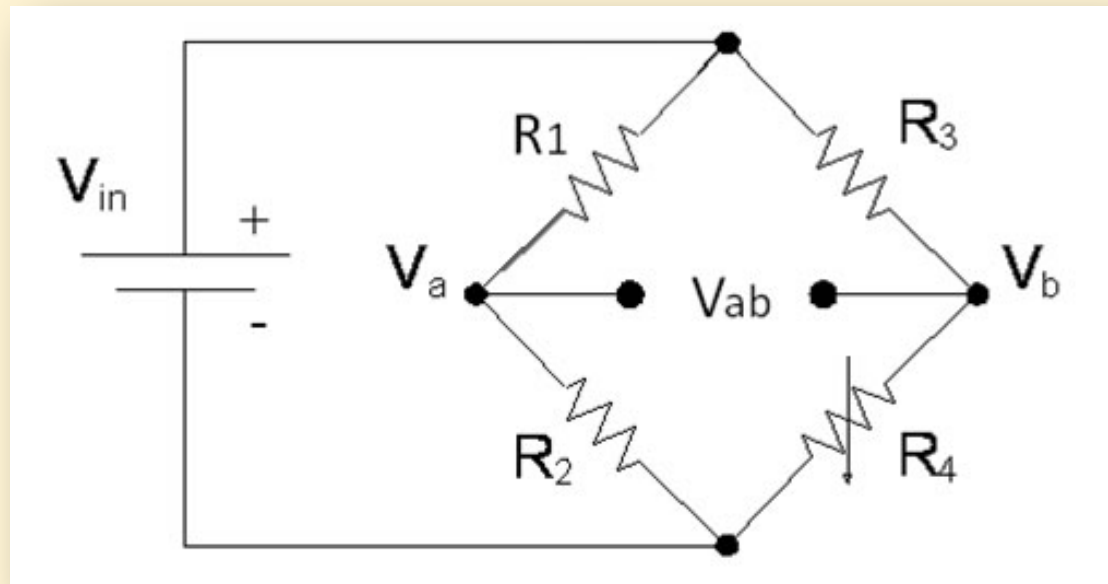
# Wheatstone Bridge and Difference Voltage


This figure shows the schematic circuit diagram of a Wheatstone bridge. The resistor pair  $R_1$  and  $R_2$  is a *resistive voltage divider* and resistors  $R_3$  and  $R_4$  form another voltage divider in parallel with  $R_1$  and  $R_2$ .



*Wheatstone bridge with one variable resistor*
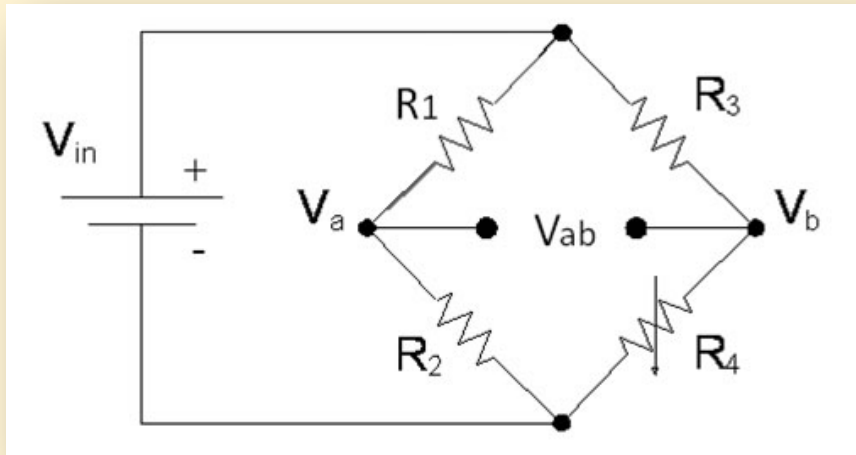
# Wheatstone Bridge and Difference Voltage cont...

The circuit is sensitive to the difference in voltage between node-**a** and node-**b**.  $V_a$  and  $V_b$  can be explained by:



*Wheatstone bridge with one variable resistor*

$$V_a = \frac{R_2}{R_1 + R_2} V_{in}$$

$$V_b = \frac{R_4}{R_3 + R_4} V_{in}$$

$$V_a - V_b = V_{ab} = \left( \frac{R_2}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right) V_{in}$$




# Wheatstone Bridge and Difference Voltage cont...

- ❖ Bridge is balanced when  $V_{ab} = 0$  volts
- ❖ This occurs when  $R_1/R_2 = R_3/R_4$
- ❖ In a typical sensing device, a variable resistor  $R_4$  ( $R_S$ ) is used
- ❖ Other three resistors are fixed
- ❖ Wheatstone bridge is initially balanced with all of the R's having the same resistance value by design, including  $R_S$  (the resistance of the sensing element).
- ❖ Value of  $R_S$  changes when the external environment changes thus affecting  $V_{ab}$  as

$$V_{ab} = \left( \frac{R_2}{R_1 + R_2} - \frac{R_S}{R_3 + R_S} \right) V_{in}$$
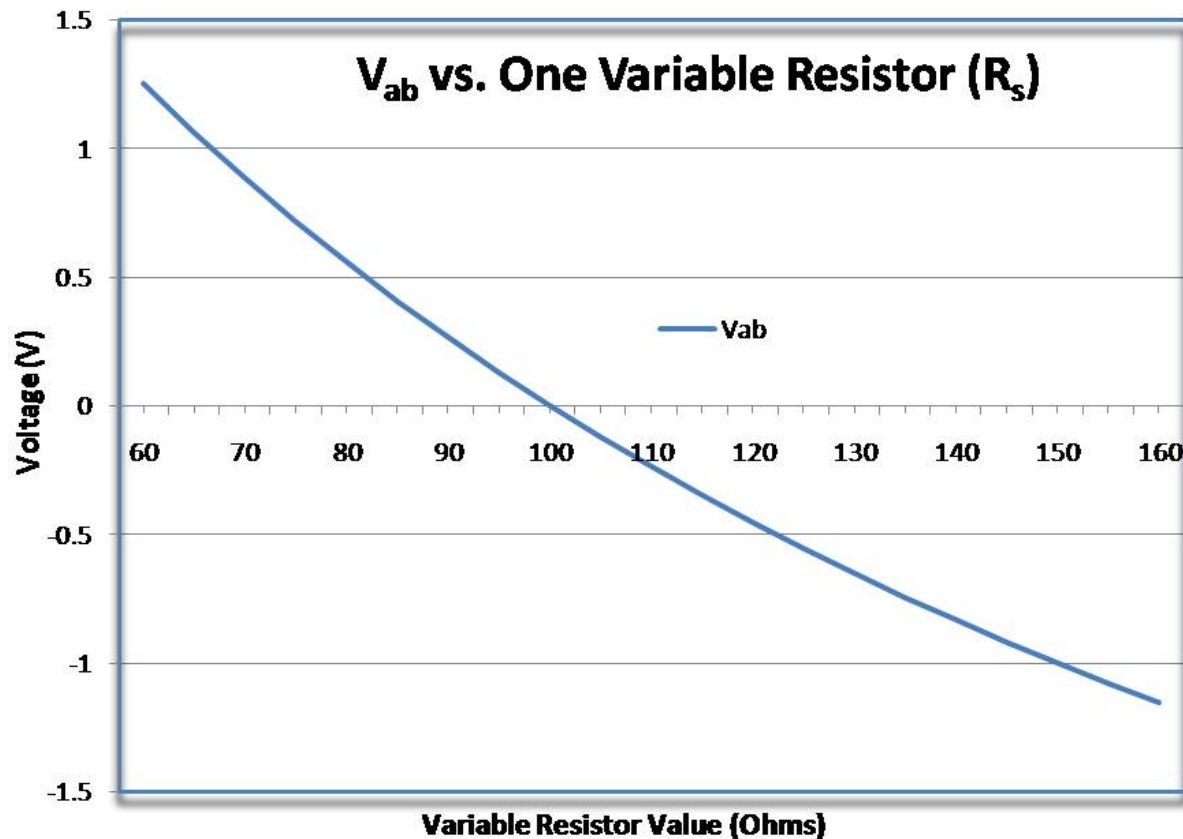
# One Variable Resistor

Assuming the transducer resistance  $R_S$  is initially  $100\ \Omega$ , and  $R_1 = R_2 = R_3 = 100\ \Omega$ , then  $V_{ab}$  can be plotted versus  $R_S$ .



Bridge is balanced when

$$R_S = 100\ \Omega$$

$$V_{ab} = 0\ \text{volts}$$


Changes in the environment affects resistance creating an unbalanced bridge

This results in a voltage proportional to resistance change
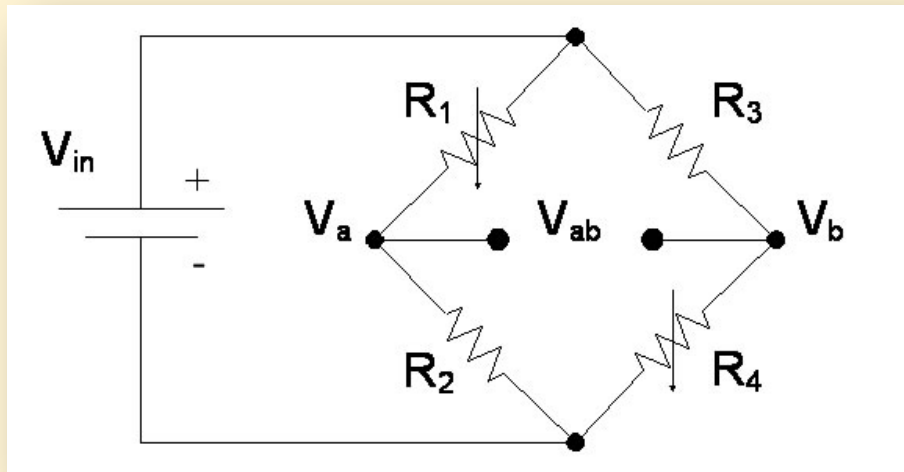
# Two Variable Resistors

Adding another variable resistor results in a more sensitive circuit

Where  $R_1$  and  $R_4$  are both variable resistors




*Wheatstone bridge with two variable resistors*

If the  $R_1$  and  $R_4$  resistors are both variable and react in the same manner to an external environmental change, then the effect on the output voltage,  $V_{ab}$  is multiplied!

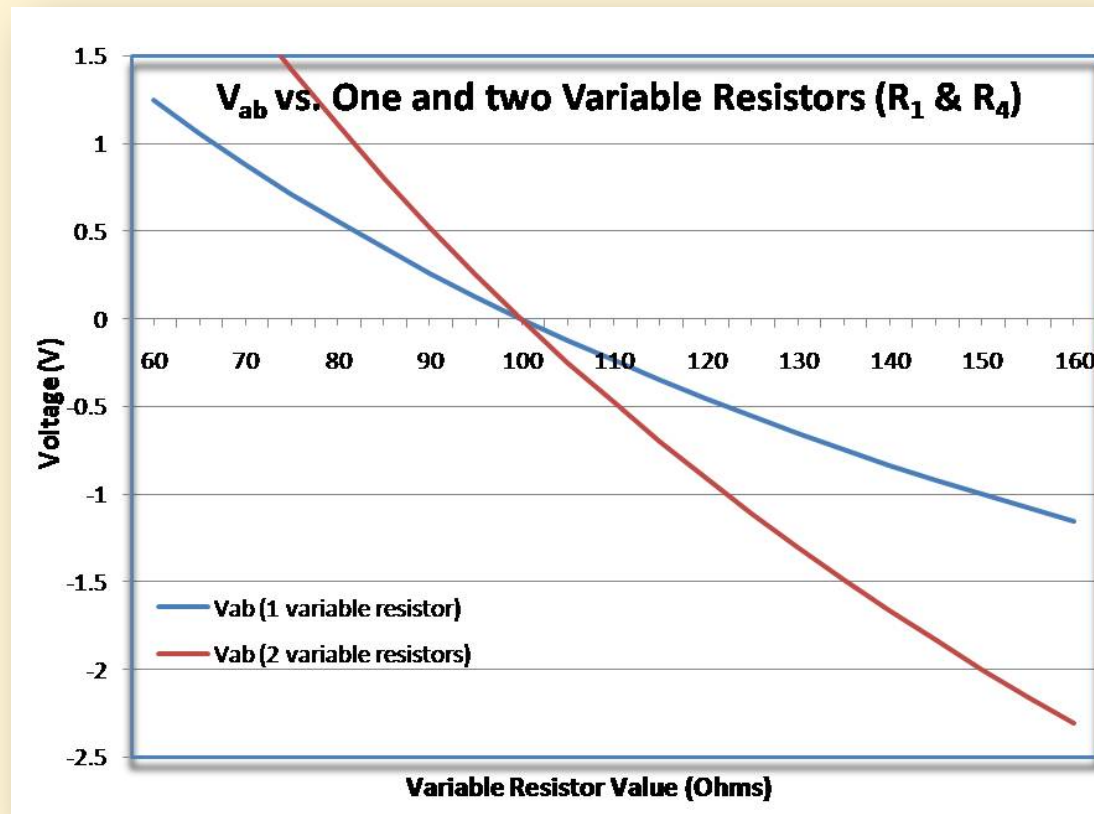
# Two Variable Resistors

Graphing  $V_{ab}$  as a function of the variable resistances of  $R_1$  and  $R_4$  (in this case changing by the same amount while the other two,  $R_2$  and  $R_3$  remain constant at  $100\Omega$ ) results in the following graph.



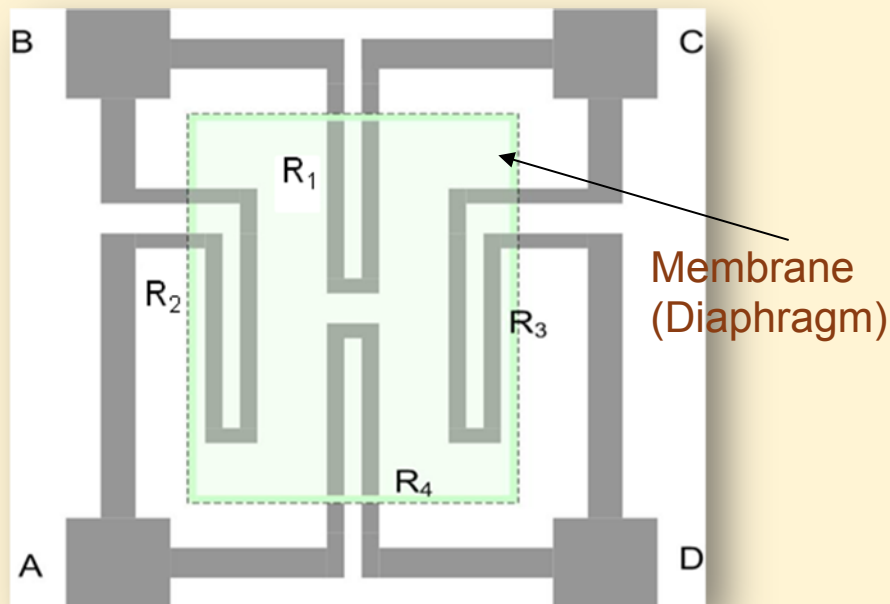
# Wheatstone Bridge as a Micro Pressure Sensor

When the Wheatstone bridge is used in a micro pressure sensor, the resistors are oriented such that  $R_1$  and  $R_4$  are variable under the stress of a flexible membrane on which they are made.



*Wheatstone bridge as a Pressure Sensor*

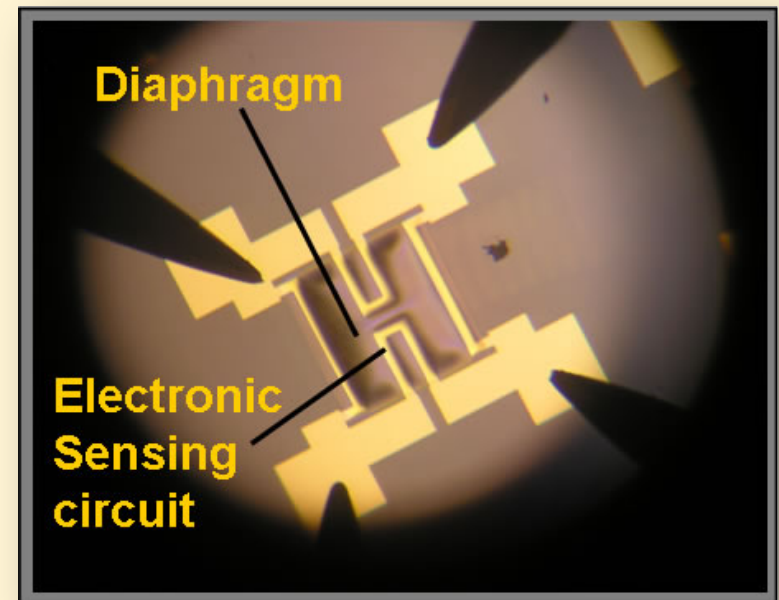

*Micro Pressure Sensor illustrating the Wheatstone bridge and the Silicon Nitride Membrane (Diaphragm)*

# Calibration

- ❖ To calibrate a Wheatstone bridge as a pressure transducer, a series of known pressure differences is applied to the sensing element(s).
- ❖ The output voltage ( $V_{ab}$ ) is measured using a voltmeter
- ❖  $V_{ab}$  versus pressure is plotted
- ❖ When an unknown pressure is applied and the output voltage read, the calibration curve of  $V_{ab}$  vs. *Pressure* can be used to determine the actual pressure.

# Summary

- ❖ Wheatstone bridge is a simple circuit used to measure transducer responses by measuring changes in voltage.
- ❖ Basic circuit analysis is used to determine the resistance when the bridge is balanced.
- ❖ Any changes in transducer resistance cause the bridge to be unbalanced providing a voltage roughly proportional to the change in resistance and corresponding to the change in pressure.
- ❖ A voltmeter measures the output of the Wheatstone bridge which can be equated to a corresponding pressure.
- ❖ In a micro pressure sensor where the Wheatstone bridge is the sensing circuit, its output can be amplified and processed to send information or to initiate a mechanical response.

# Acknowledgements

Made possible through grants from the National Science Foundation Department of Undergraduate Education #0830384, 0902411, and 1205138.

Any opinions, findings and conclusions or recommendations expressed in this material are those of the authors and creators, and do not necessarily reflect the views of the National Science Foundation.

Southwest Center for Microsystems Education (SCME) NSF ATE Center  
© 2012 Regents of the University of New Mexico

Content is protected by the CC Attribution Non-Commercial Share Alike license.

Website: [www.scme-nm.org](http://www.scme-nm.org)